

Cheat wiring to connect RS-232 to RS-422 without using an adapter

Here is a way to bypass the B & B electronics converter, the 422LPCON. This would be used to connect two pieces of differing equipment.

Remember, this is good for short distances only, possibly 10 feet or so.

As wired, this connection is bi-directional.

