

Selecting and Using RS-232, RS-422, and RS-485 Serial Data Standards

Three common serial data standards: RS-232, RS-422, and RS-485 are described by specification and electrical interface. Cable termination techniques, use of multiple loads, daisy-chaining of RS-232, conversion of RS-232 to RS-485, converting RS-485 to RS-232, and RS-232 port powered RS-485 conversions are described.

"The great thing about standards is there are so many to choose from." This statement was made at a recent conference on fiber optics, and it holds true for electrical-interface standards as well. Serial-data standards tend to evolve separately, within particular industries, thus we have more standards than we should.

Perhaps the most successful serial-data standard for PC and telecom applications is the RS-232. Similarly, the RS-485 and RS-422 are among the most successful standards for industrial applications. These standards are not directly compatible, however for purposes of control and instrumentation it is often necessary to communicate between them. This article offers insight into the different standards (electrical physical-layer specifications), how to convert from one standard to another standard, and how to combine different standards within the same application.

The RS-232 link was initially intended to support modem and printer applications on IBM PCs, however it now enables a variety of peripherals to communicate with PCs. The RS-232 standard was defined as a single-ended standard for increasing serial-communication distances at low baud rates (< 20kbps). Over the years the standard has changed as necessary to accommodate faster drivers like the MAX3225E, which offers 1Mbps data-rate capability. For RS-232 compliance, a transceiver such as the MAX3225E must meet the electrical specifications listed in Table 1. A typical connection (Figure 1) shows the use of hardware handshaking to control the flow of data.

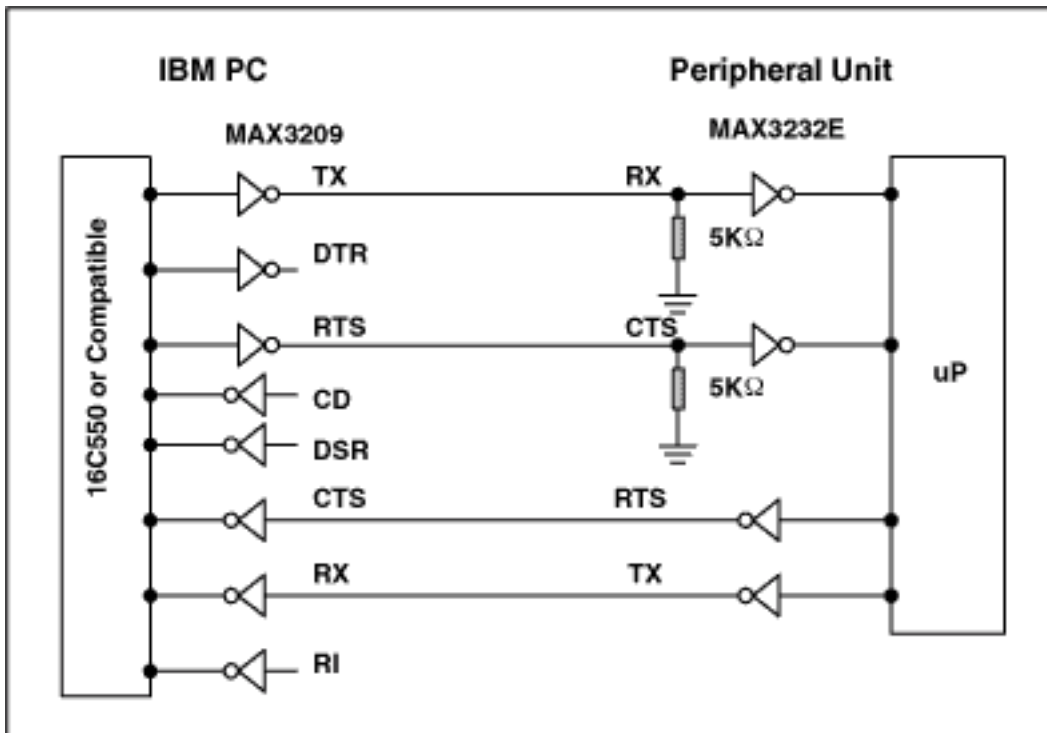


Figure 1. Typical RS-232 connection.

A typical RS-232 signal (Figure 2, CH1) swings positive and negative; note the relative location of the 0V trace markers on the left axis. Although the RS-232 data is inverted, an overall translation from TTL/CMOS to RS-232 and back to TTL/CMOS restores the data's original polarity. Typical RS-232 transmissions seldomly exceed 100 feet for two reasons: The difference between transmitted levels ($\pm 5V$) and receive levels ($\pm 3V$) allows for only 2V of common-mode rejection, and the distributed capacitance of a longer cable can degrade slew rates by exceeding the maximum specified load (2500pF). Since the RS-232 was designed as a point-to-point rather than multi-drop interface, its drivers are specified for single loads from $3k\Omega$ to $7k\Omega$. Therefore, a daisy-chain scheme is typically implemented for multi-drop interface applications (Figure 3).

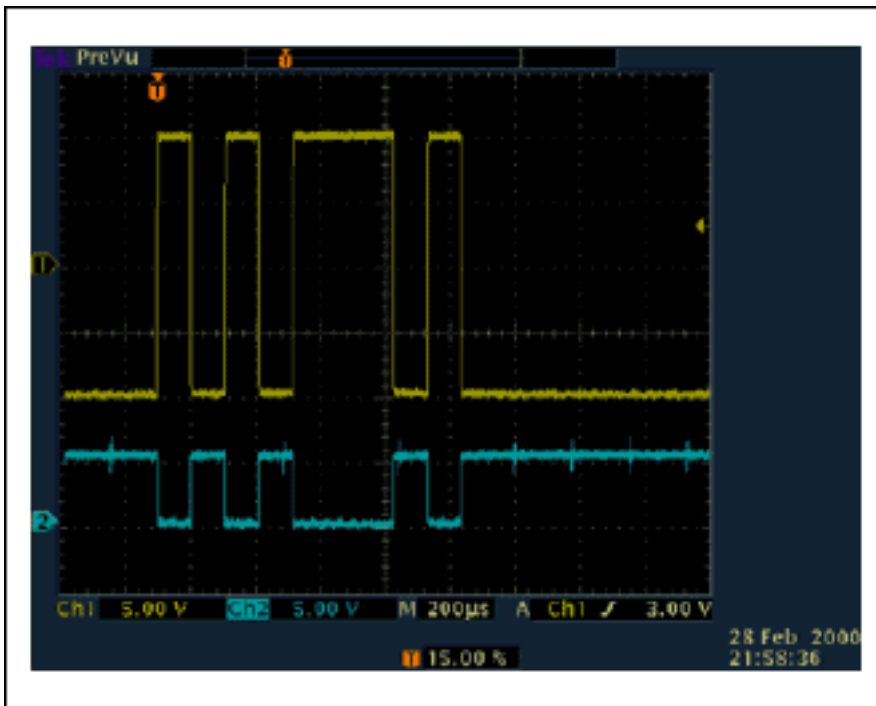


Figure 2. An RS-232 receiver accepts the bipolar input signal (top trace, CH1) and outputs an inverted TTL/CMOS signal (bottom trace, CH2).

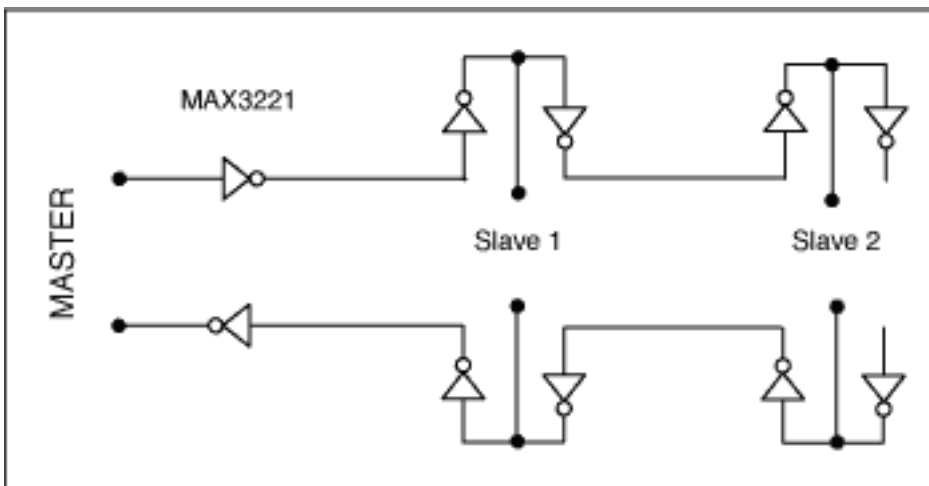


Figure 3. Daisy-chaining allows multiple slave transceivers on a single RS-232 line.

Daisy-Chain Devices

In a daisy-chain configuration, the RS-232 signal enters through one receiver and is looped through to a transmitter. This configuration is repeated for subsequent devices along the data transmission line. Cable breaks are a major problem with this technique. A break between slave 1 and slave 2, prevents all downstream devices from transmitting or receiving data. Other multi-drop RS-232 techniques involve pre-buffering or boosting the RS-232 output drive (enabling it to drive multiple $5k\Omega$ inputs in parallel).

To eliminate the problems associated Daisy-Chain networks Maxim developed the MAX3322E/MAX3323E, which are specifically designed to be configured in multi-drop applications. These unique devices employ a logically switched input resistance of $5k\Omega$. When a

device is not selected, its input resistance remains in a high impedance state allowing communication to proceed with other devices along the shared bus.

Another solution would be to convert the RS-232 RX and TX signals to an RS-422 signal (see Table 2). RS-422 is a differential standard that allows transmission over much greater distances. The higher input resistance of RS-422 inputs, combined with their higher drive capability, allows a connection of up to 10 nodes (Figure 4). Another advantage of RS-422 is the separate transmit and receive paths, for which no direction control is needed. Any necessary handshaking between devices can be performed with either software (XON/OFF handshaking) or hardware (a separate set of twisted pairs). The MAX3162 provides an economical way to translate between RS-232 and RS-422 signals. For more detail, refer to the section titled "RS-232/RS-485 Protocol Translators".

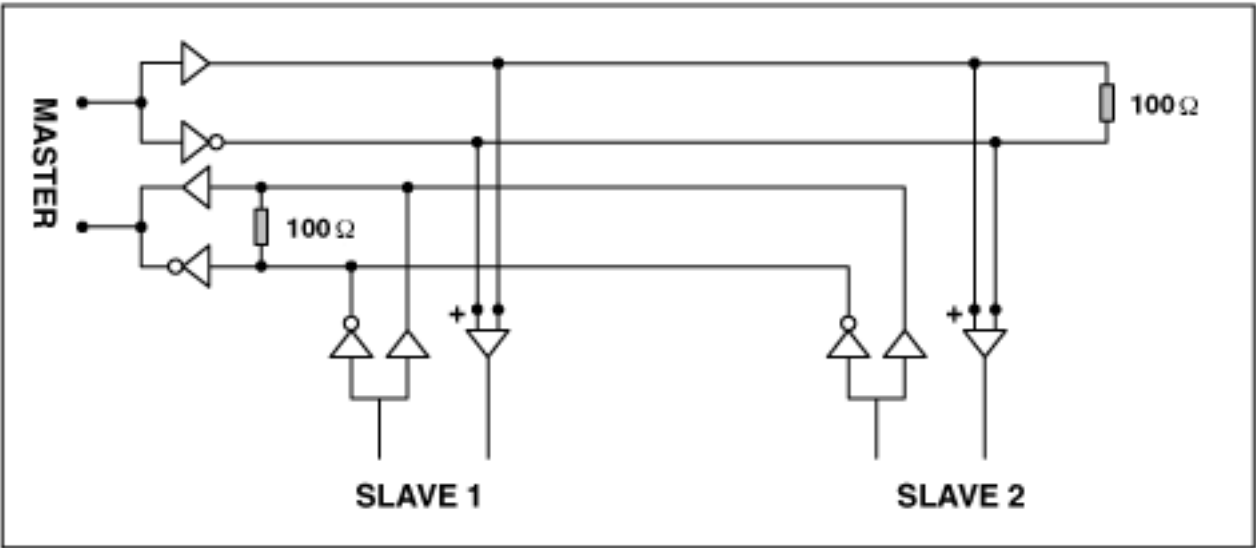


Figure 4. A typical RS-422 system allows as many as 10 slave transceivers on the differential transmission line.

RS-422 and RS-485 transceivers are often confused with each other; one is assumed to be a full-duplex version of the other. However the electrical differences in their common-mode ranges and receiver-input resistances suit these standards for different applications. Since the RS-485 meets all of the RS-422 specifications (Table 3), RS-485 drivers can be used in RS-422 applications. The opposite, however, is not true. The common-mode output range for RS-485 drivers is -7V to +12V, where as the common-mode range for RS-422 drivers is only $\pm 3V$. The minimum receiver-input resistance is $4k\Omega$ for RS-422 drivers and $12k\Omega$ for RS-485 drivers.

Table 1. RS-232 Summary of Major Electrical Specifications

Parameter	Conditions	Min	Max	Units
Driver Output Voltage Open Circuit			25	V
Driver Output Voltage Loaded	$3k\Omega < R_L < 7k\Omega$	± 5	± 15	V
Driver Output Resistance Power Off	$-2V < V < 2V$		300	

Slew Rate		4	30	V/ μ S
Maximum Load Capacitance			2500	pF
Receiver Input Resistance		3	7	k Ω
Receiver Input Threshold:				
Output = Mark (Logic 1)		-3		V
Output = Space (Logic 0)			3	V

Table 2. RS-422 Summary of Key Specifications

Parameter	Conditions	Min	Max	Units
Driver Output Voltage Open Circuit			± 10	V
Driver Output Voltage Loaded	$R_L = 100\Omega$	2 -2		V
Driver Output Resistance	A to B		100	Ω
Driver Output Short Circuit Current	Per output to common		150	mA
Driver Output Rise Time	$R_L = 100\Omega$		10	% of bit width
Driver Common-Mode Voltage	$R_L = 100\Omega$		± 3	V
Receiver Sensitivity	$V_{CM} \leq \pm 7V$		± 200	mV
Receiver Common-Mode Voltage Range		-7	7	V
Receiver Input Resistance		4		k Ω
Differential Receiver Voltage	Operational		± 10	V
	Withstand		± 12	V

Table 3. RS-485 Summary of Key Specifications

Parameter	Conditions	Min	Max	Units
Driver Output Voltage Open Circuit		1.5 -1.5	6 -6	V V
Driver Output Voltage Loaded	$R_L = 100\Omega$	1.5 -1.5	5 -5	V V
Driver Output Short Circuit Current	Per output to common		± 250	mA
Driver Output Rise Time	$R_L = 54\Omega$ $C_L = 50pF$		30	% of bit width
Driver Common-Mode Voltage	$R_L = 54\Omega$		± 3	V
Receiver Sensitivity	$-7V < V_{CM} < 12V$		± 200	mV
Receiver Common-Mode Voltage Range		-7	12	V
Receiver Input Resistance		12		k Ω

To reduce wiring expense and achieve longer line lengths, RS-485 transceivers have become a popular standard for use in point-of-sale, industrial, and telecom applications. Its wider common-mode range also enables longer line lengths and a higher input resistance per node, allowing more nodes to be connected to the bus (Figure 5).

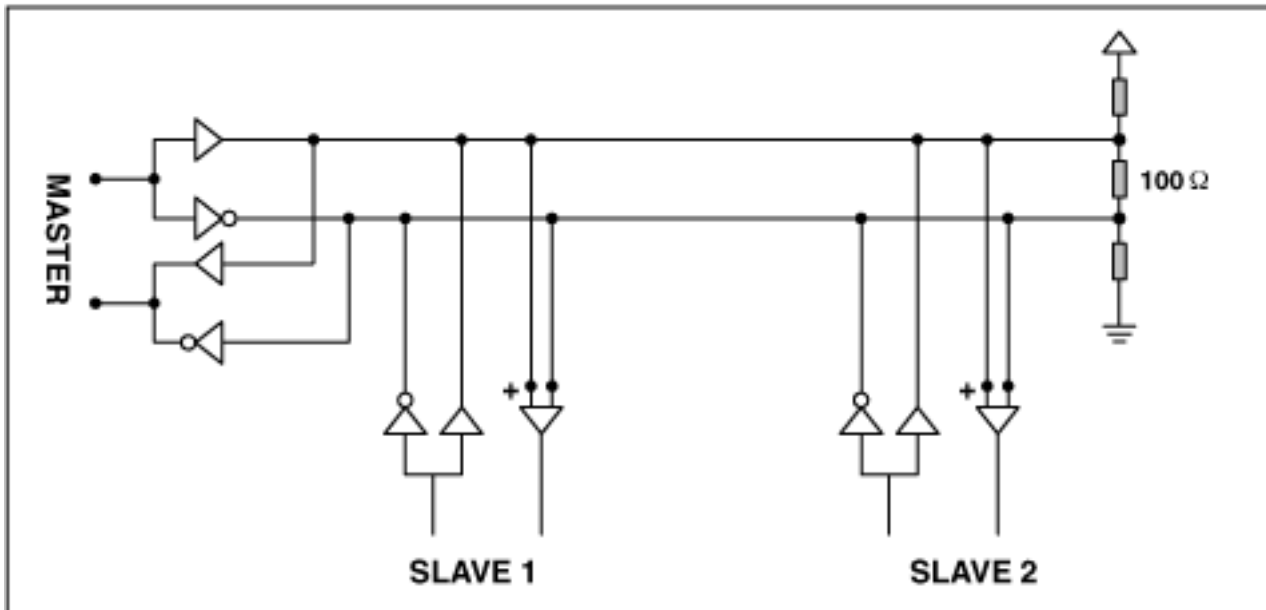


Figure 5. Compared with RS-422, the higher input impedance and wider common-mode range of an RS-485 connection enables longer line lengths.

Differential RS-485 transmissions (Figure 6) produce opposing currents and magnetic fields along each segment (wire) of a twisted-pair cable; thus minimizing the emitted electromagnetic interference (EMI) via cross-canceling of the opposing fields around each wire. For transmissions through a long cable or at high data rates, the cable appears as a transmission line and should be terminated with the cable's characteristic impedance. This aspect of the RS-485 connection causes confusion. Does the line need to be terminated, and if so how should it be terminated? If the designer is not the end user, should these questions be left for the installer to figure out? For most RS-485 transceivers, the data sheet indicates a simple choice between no termination, and a simple point-to-point termination when the cable acts as a transmission line (Figure 7). A termination resistor across the A-B terminals is harmless. By default, the transmission line should be terminated at the last transceiver on the line (bus).

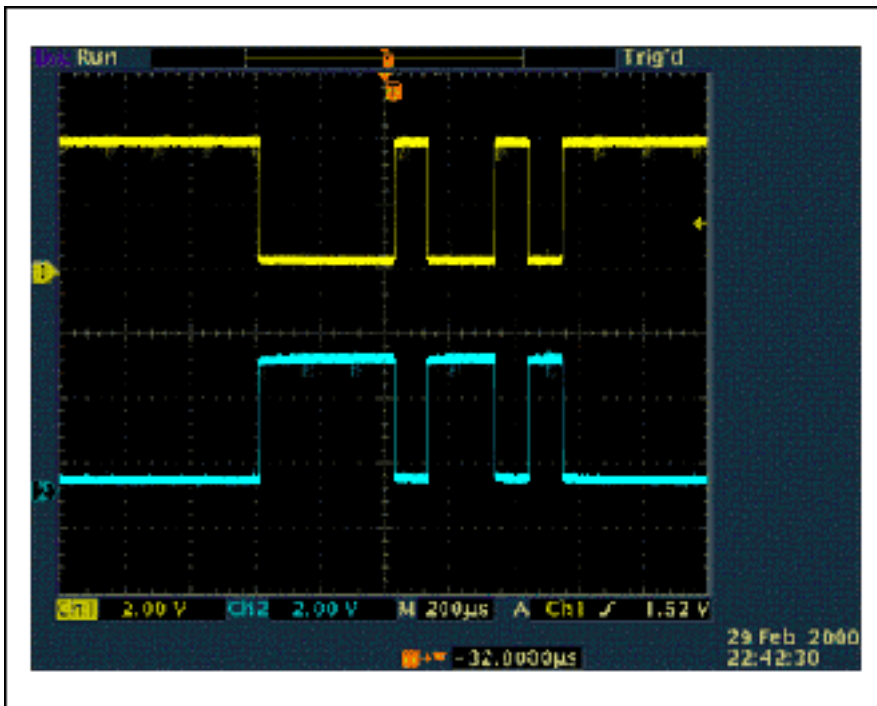


Figure 6. The opposite-polarity signals on an RS-485 line minimize EMI by cross-canceling each other's respective magnetic fields. The GND references on the above scope photo have been shifted (offset) to clearly show the inverted polarities of the RS-485 output signals.

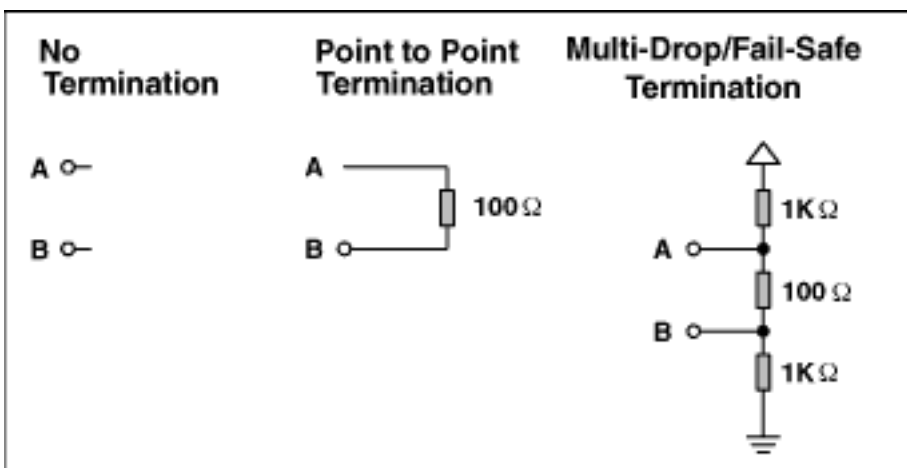


Figure 7. The choice of termination resistors for a transmission line depends on the application.

Fail-Safe


Deciding whether you need a termination resistor or not is only part of the problem in implementing an RS-485 system. Normally, an RS-485 receiver output is "1" if $A > B$ by +200mV or more, and "0" if $B > A$ by 200mV or more. In a half-duplex RS-485 network, the master transceiver tri-states the bus after transmitting a message to the slaves. Then, with no signal driving the bus, the receiver's output state is undefined, for the difference between A and B tends towards 0V. If the receiver output (RO) is "0", the slaves interpret it as a new start bit and attempts to read the following byte. The result is a framing error, because the stop bit never occurs. The bus goes unclaimed, and the network stalls.

Unfortunately, different runs of chips can produce different output signals on RO for a 0V

differential input. The prototype can work perfectly, however certain nodes will fail in a later production run. To solve this problem, bias the bus as shown in Figure 7 (Multi-Drop/Fail-Safe Termination). Biasing the bus ensures that the receiver output remains "1" when the bus is tri-stated. Or, you can use "True Fail-Safe" receivers like those of the MAX3080 (5V) and MAX3070 (3V) families. These devices ensure an RO output of "1" in response to a 0V differential input by changing the receiver's threshold to -50mV.

RS-232/RS-485 Protocol Translators

The MAX3162 is a very unique device for it contains both RS-232 and RS-485 receivers and transmitters. This wide range of communication devices contained within a single device enables an individual to convert bi-directionally between RS-232 and RS-485 signals. The circuit in Figure 8 illustrates the MAX3162 configured to bi-directionally convert RS-232 and RS-485 signals in a point-to-point application.

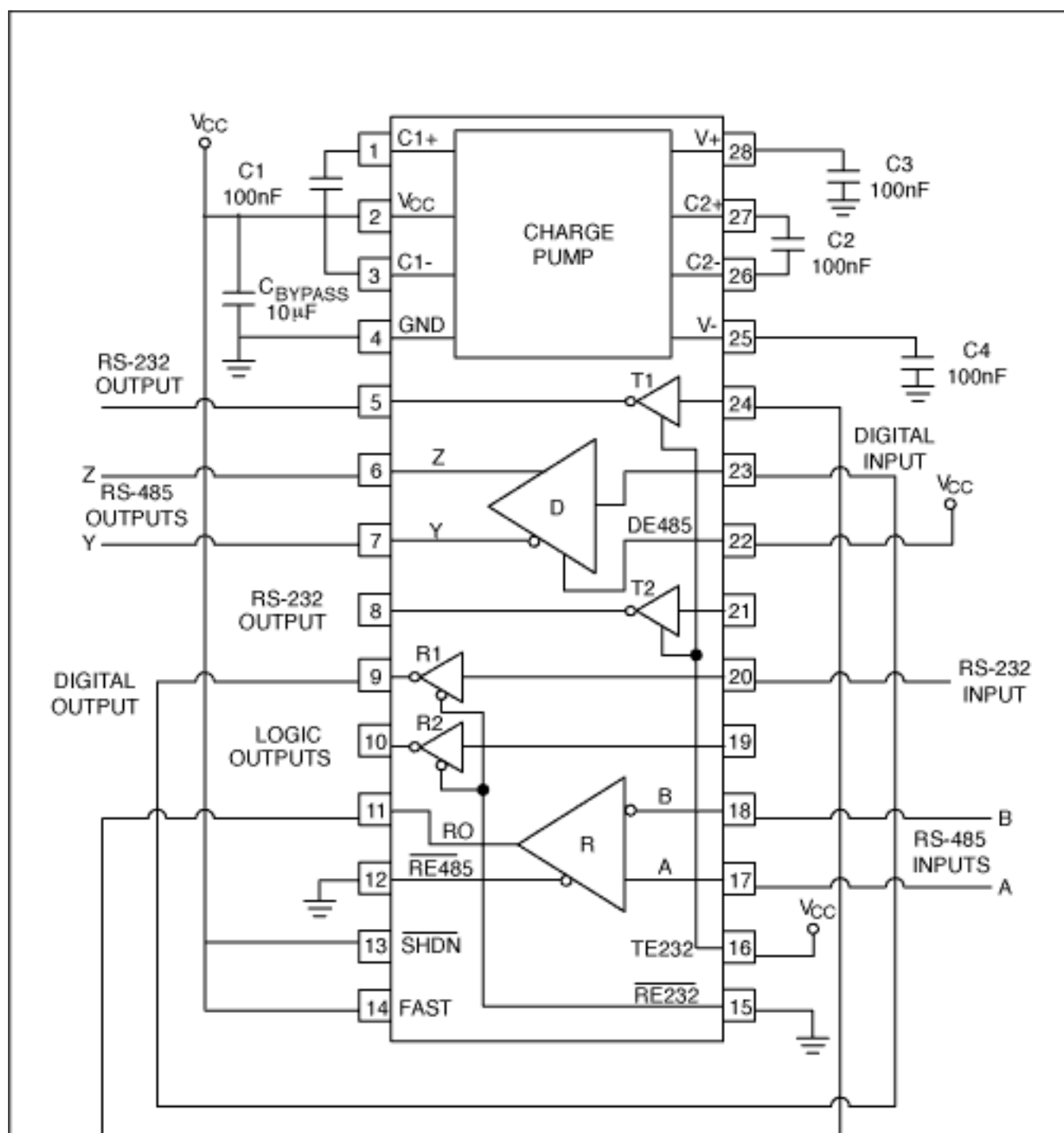

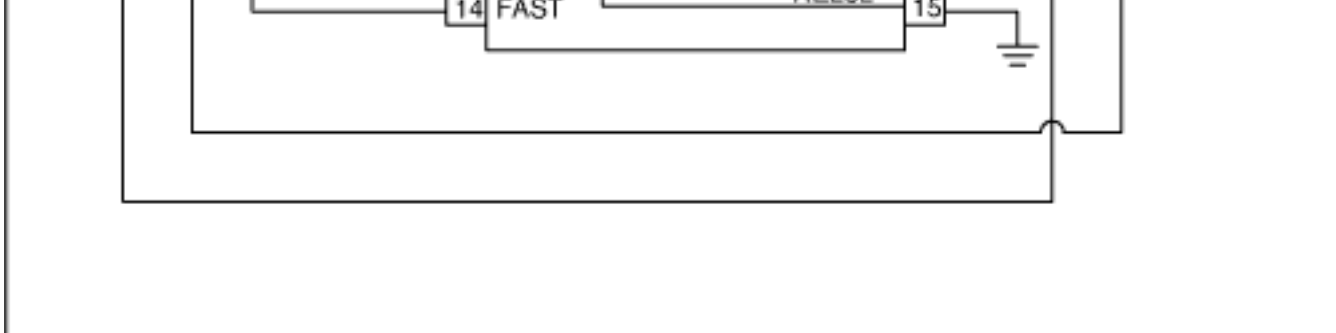


Figure 8. The above figure utilizes the MAX3162 to convert bi-directionally between RS-232 and RS-485 signals in a point-to-point application.

Figure 9 shows the MAX3162 configured as an RS-232/RS-485 multi-point protocol translator. The direction of translation is controlled through the RTS signal R1IN. The single-ended RS-232 receiver input signal is translated to a differential RS-485 transmitter output. Similarly, a differential RS-485 receiver input signal is translated to a single-ended RS-232 transmitter output. RS-232 data received on R2IN is transmitted as an RS-485 signal on Z and Y. RS-485 signals received on A and B are transmitted as an RS-232 signal on T1OUT.

The RTS line offers a common means for controlling bus direction in circuits that convert from RS-232 to RS-485. This line on the RS-232 port controls whether the RS-485 transceiver acts as a transmitter or a receiver (Figure 9). Note that the system cannot be sure that a byte of data in the UART's transmit buffer has been transmitted unless the system monitors the RS-485 driver input (DI). That is, the system must either allow for a fixed time delay or actively monitor the DI input before using the DE input to change the bus direction.

Other direction-control techniques include using a microcontroller and driving the DE input with data while pulling the A-B lines apart (connecting a pull-up resistor from A to 5V and connecting a pull-down resistor from B to ground). The value of these resistors varies with cable capacitance, but is typically 1k Ω .

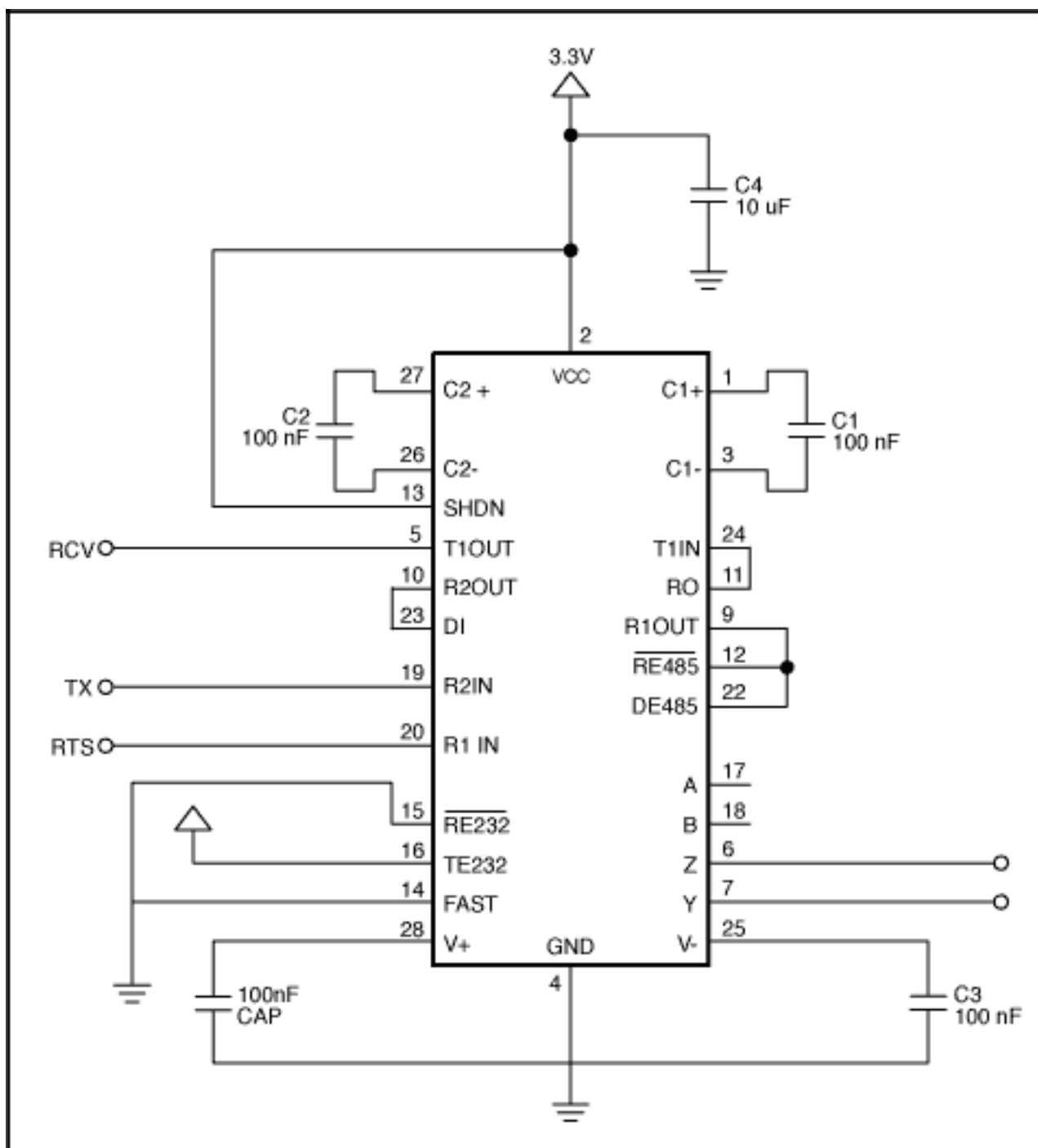


Figure 9. The above figure utilizes the MAX3162 to convert bi-directionally between RS-232 and RS-485 signals in a multi-point application.

Port-Powered Devices

Many converters from RS-232 to RS-485 are "port-powered converters", in which the RS-485 power is derived from the RS-232 RTS line (or sometimes a combination of the RTS and CTS (DTR) lines). Since the power available from an RS-232 port is limited, the RS-485 launch voltages are not achieved when using a port-powered converter with for example 100 RS-485 terminations. However, the low receiver threshold (200mV) allows for a fair margin for error. This technique is acceptable in systems with short line lengths and without termination resistors across the A-B terminals.

Hot-Swap

When circuit boards are inserted into a hot or powered backplane, differential disturbances to the data bus can lead to data errors. Upon initial circuit board insertion, the data communication processor undergoes its own power-up sequence. During this period, the processor's logic-output drivers are high impedance and are unable to drive the DE and /RE\ inputs of the MAX3060E/MAX3080E to a defined logic level. Leakage currents up to $\pm 10\text{mA}$ from the high-impedance state of the processor's logic drivers could cause standard CMOS enable inputs of a transceiver to drift to an incorrect logic level. Additionally, parasitic circuit board capacitance could cause coupling of VCC or GND to the enable inputs. Without the hot-swap capability, these factors could improperly enable a transceiver's driver or receiver.

References

1. RS-422 and RS-485 Application Note, B&B Electronics (This is a great source of information on RS-232, RS-485 and RS-422 standards and their practical realizations. <http://www.bb-elec.com>)
2. Serial Port Complete, Jan Axelson (This definitive reference for serial ports includes lots of useful source code written in Visual Basic. <http://www.lvr.com>)

More Information

MAX232: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX3162: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX3232: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX485: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)